

Lab Overview

In this lab assignment, you will do the following:

- Learn how to use an assembler and simulator/debugger. Start using the 8051 and ARM processors.
- Learn how to use the WinCUPL/WinSim design suite for the Atmel AT16V8C SPLD.
- Plan the layout of your development board and obtain your parts kit.
- Start learning schematic capture and gain skills in soldering. Build your basic hardware.

The Part 1 Elements of this lab assignment should be done (flexible date) by **Friday, Sept. 8, 2023**.

The Part 2 Elements of this lab assignment must be done by **Friday, Sept. 15, 2023**.

The Part 3 Elements and signature due date for the entire lab assignment is **Friday, Sept. 22, 2023**.

The final submission due date (when all files must be turned in) is **11:59pm Sunday, Sept. 24, 2023**.

The cutoff date for this lab is **Saturday, Sept. 30, 2023**.

Students can collaborate on Lab #1 but must individually develop their own unique hardware and software. This lab is easier than the following labs and it is weighted as a small part of your course grade. This gives you a chance to come up to speed on basic hardware and firmware concepts, to make sure that you have all the parts you need to do the assignment, and to make sure that you have access to the lab and the lab equipment is all functional. **The following lab assignments will be more involved and more time consuming, so you will have to plan your time wisely.**

Lab Details

1. Review Homework assignments #1 and #2, which are associated with Lab #1.
2. Obtain lab access. If you do not already have one, obtain a Buff OneCard, needed for access to the engineering center and the 1B28 laboratory. Continuing Education students not seeking a degree can obtain a card for ~\$30. For more information, see <https://www.colorado.edu/buffonecard/>. **Please get your card ASAP, and follow current Department processes for obtaining access to our lab.**
3. For the first part of this lab, you will need to use an 8051 assembler and simulator/debugger of your choice. The recommended options are the ASM51 assembler and Emily52 simulator (these are bundled together in a demo kit in a self-extracting .exe file) or **using the Silabs EFM8BB1 dev board with Simplicity Studio**. Other options include the AS31 or ASX51 assemblers. You may use the tools installed on the computers in the lab, or you can obtain your own copy from the course website. Refer to the assembler homework assignments (HW #1 & #2) for more information.

Note: You may need to use an emulator like DOSBox in order to install and run DOS-based tools in 64-bit environments. If you're running 64-bit Windows, go to www.dosbox.com and download for Windows OS. This is an x86 emulator which will run in Windows x64. Create two directories with their corresponding files in the C: directory – you'll have a Dosbox folder and an Emily52 folder. Run the dosbox executable and the Z: prompt will come up. Follow these steps:

```
Z:\> mount c c:\emily52
Z:\> C:
C:\> emily52.exe filename.hex /overlap
```

Emily52 is now running in a x86 emulator.

DOSBox will truncate filenames that are too long, so you may not be able to differentiate between longfilename_v1.asm and longfilename_v2.asm for example. DOSBox is also case insensitive and may have issues with file paths with spaces in them.

See Homework #2 and the Assembly Language and Emily52 overview documents available on the course web site. We do not intend to spend too much time on these older tools this semester.

NOTE: Students are encouraged to use the EFM8 dev board and its development environment to develop and demonstrate their program using breakpoints. Students who use the EFM8 to fully demo their code do not need to use or demonstrate the older Emily52 or EdSim51 simulators.

1. Write a single assembly language program which meets the requirements below.

This program shall calculate the following equation using integer division: $Z = (X)/(Y*4)$
In this assignment, X, Y, and Z are unsigned 8-bit values.

Example: If $X=0x40$ and $Y=0x03$, then $Z=0x05$. [64 div 12 = 5 with remainder 4]

Preconditions:

- Accumulator contains value of X. B register contains the value of Y.

Post Conditions:

- Internal data memory (IRAM) location 0x20 contains the value of (X)
- IRAM location 0x21 contains the value of (X)
- IRAM location 0x22 contains the value of (Y)
- IRAM location 0x23 contains the value of (Y*4)
- IRAM location 0x24 contains Z, the 8-bit quotient (in hexadecimal)
- IRAM location 0x25 contains the 8-bit remainder (in hexadecimal)
- IRAM location 0x30 contains the error code.

Other requirements:

- This program must implement an algorithm that does not use the 8051 divide (DIV) or multiply (MUL) instructions.
- Use an 8051 shift/rotate instruction to implement the multiplication.
- The program must start at address 0000h.
- When the calculation is complete, the program jumps to a label named 'ENDLOOP' and enters an infinite loop.

Error handling:

- If no error occurs during program execution, the program shall write a '0x00' into the error code in internal memory.
- If the divisor is 0, then the program shall write a '0x01' into the error code in internal memory and then immediately jump to 'ENDLOOP' without performing any calculations
- If the calculation exceeds an 8-bit value when multiplying, then the program shall write a '0x02' into the error code in internal memory and then immediately jump to 'ENDLOOP' without performing any further calculations.

Implementation suggestions:

- Refer to the test1.asm & test3.asm files distributed with Emily52 for simple program examples.
- Implement your code in stages. One possibility for this type of incremental development is:
 - i. Stage 1: First, implement the program using the DIV instruction and do not include any error handling.
 - ii. Stage 2: Once that is working, replace the DIV instruction with your algorithm.
 - iii. Stage 3: After that is working, add the instructions necessary to implement the required error handling.

Test your program with a simulator by setting the accumulator and B register to various initial values.

Note: Use a combined code and data space in the 8051 (/overlay option in Emily52). Practice using the various capabilities of the simulator/debugger that you have chosen to use.

During the demo, the TA will have you test the results for various values of dividend and divisor (either using the simulator or debugger). Make sure your program can correctly handle different starting values.

- **Submit your final commented firmware.** During signoff, show the TA your code and .LST file.

2. Read the final project assignment and discuss your questions with the TA during the Part 1+2 signoff.
3. For the SPLD design suite part, you will need the Atmel WinCUPL tools, which are available on the Microchip web site and through a link on our course web site. These tools are also installed on the computers in our lab. Learn how to use Microchip (Atmel) WinCUPL and WinSim. Review the tutorials and example code available on the course web site. Focus on learning the basics of these tools only, as they are not a primary element of this course.
4. Using WinCUPL, develop code for the Atmel AT16V8C SPLD. Assign A15, A14, A13, A12, /RD, and /PSEN from the processor to six of the SPLD inputs. Generate two outputs:
/READ = /RD & /PSEN, and /CSPERIPH = !(A15 & A14 & A13 & A12).

Verify your logic with WinSim, using at least six test vectors to show correct logic functionality for a well-chosen subset of all possible input conditions. The /READ output of the SPLD should be toggling when either /RD or /PSEN toggles. The /CSPERIPH OUTPUT should be high most of the time, and should be low only for addresses in the range of F000h-FFFFh.

- As part of the signoff procedure, show the TA your commented .PLD source file and .SI simulator input file. Explain how these files are structured.
- Note: Students are allowed to use discrete logic in their hardware implementation if they prefer that solution over the SPLD.

COMPLETE ALL THE ITEMS ABOVE FOR THE PART 1 ELEMENTS CHECKPOINT.

PART 2 ELEMENTS

5. Obtain a parts kit for the lab. The TA's will make these available for purchase.
 - Payment may be made via Venmo, PayPal, or cash. If paying electronically, add any service charges and fees to the amount that you pay.
 - Upon receiving the kit, check to make sure all items are present and contact the TA's right away if any parts are missing. The parts kit contents list is posted on the course web site.
 - Wire wrap wire may be obtained in the laboratory. Please only take what is required to implement your microcontroller board (please only take 2-3 yards of each color needed at a time).
 - Soldering irons and solder will be available to use in the laboratory.
 - **Please leave the lab equipment in the lab, make sure to turn off the soldering irons, and make sure the door to the lab is closed and locked when you leave.**
 - You may sign out a tool kit with wire wrap tool, cutters, needle nose mini-pliers, power supply, 28-pin ZIF socket, NVRAM, and RS-232 cable for the semester. You may also sign out items such as a portable logic analyzer, digital logic probe, high frequency oscilloscope probe, dev kits, etc.
Take good care of these items, as you are financially responsible for them.
6. If you don't have experience with soldering electronics, read the article "A Guide to Better Soldering", available in the lab or visit a web site (e.g. YouTube or Metcal) and read about soldering techniques and tips. Answer the following questions for yourself:
 - Why is flux used? What type of flux should be used with electronic circuits? Will flux remove grease from a connection point?
 - What is a cold solder joint, and how is it created?
7. [Optional] Skim the article "Handling of Power Plastic Transistors", available on the course web site. You should always take care not to stress the pins or packaging of any electronics.
8. You will be using the 6"x8" printed circuit board (PCB) from your parts kit. Study the schematics included in the document "**ECEN 5613 PCB Layout and Partial Schematics**", which is available on the course web site. The schematics show you some of the circuit connections that are present on your PCB. Note that not all of the components shown in the partial schematics will end up being populated on your board; the components are in the schematics so that pads (through hole or surface mount) would be present in the PCB design. You will need to determine which components you will need to load during the semester.
9. Your initial hardware assignment will be to implement your core microcontroller design. The basic circuit elements consist of an 80C51 microcontroller with power-on and run-time reset circuitry and an 11.0592MHz crystal oscillator, a 7805 (or 340T5) +5V voltage regulator, and hardware, such as your PCB, standoffs, power connector, 9-pin RS-232 connector, etc.

Design your power supply circuit and draw a schematic using any tool like Orcad Capture, KiCad, Altium, or Mentor. You should include the 2.1mm power jack, power switch, the 7805 voltage regulator, and a power-on LED which glows whenever power is applied to your board. Some starter schematics are on the course web site (in OrCad .DSN and Adobe .PDF formats).

Design your oscillator circuit using the 11.0592 MHz crystal and the 27pF capacitors and add this circuit to your schematic.

Design your power-on reset circuit with run-time reset capability. Include an RC circuit and a pushbutton. You may choose to mount the pushbutton on the top or the bottom of your board.

- **Submit a PDF printout of your schematics on Canvas in the Lab 1 Part 2 Elements folder.**
- **Note: Include a PDF printout of your schematic as part of each lab submission this semester.**


COMPLETE ALL THE ITEMS ABOVE (Parts 1 & 2) FOR THE PART 2 ELEMENTS SIGNOFF.

COMPLETE ALL THE ITEMS BELOW FOR THE PART 3 ELEMENTS SIGNOFF SHEET.

10. **Before soldering in any components and before using your bare PCB, you must test to make sure that you do not have any short circuits. Using a multimeter, test between your +5V and ground connection on the PCB to verify that there is an open circuit between power and ground.** If you catch a PCB flaw at this point, you won't waste time and money debugging your board after you've added your circuits.


Study your PCB carefully and compare it to the partial schematics. Use a multimeter to learn how the power and ground planes on your board are designed. Are they connected directly to the VCC and GND pins on each chip? Are they connected directly to the VCC and GND headers distributed around the board? Which of the capacitors in the partial schematics are through hole and which are surface mount technology (SMT)?

11. Spend some time planning your layout (see the "Example Board Layout" document provided). A lot can be learned from laying out a circuit poorly, but it's usually much easier to correct an error at the layout stage of the game rather than after you have already soldered in chips and wrapped 50 wires. Try to keep your wires short to minimize noise problems. To help in development, you will probably use standoffs to support your board in its four corners. It is recommended not to drill any additional holes in your PCB, as you take the chance of damaging existing traces or shorting together the VCC and GND planes. In addition, it is suggested that you leave a keep-out area (perhaps 0.5" to 0.8" wide) around the edge of your board, so that you can add connectors or other parts later in the semester. **NOTE:** Parts to be added to your board this semester include a 32KB NVSRAM for code, (optionally) a 32KB NVRAM/SRAM for data; supporting glue logic, such as your decoding circuits, pull-up resistors and an address/data line demultiplexer; a MAX232 RS-232 line driver/receiver; 8-pin serial EEPROM, and an LCD. You need to leave room for these parts on your board.
12. Using a marker or pen, neatly print **your name** and the text "**S2023**" in the big white space on the bottom side of the PCB. This will be checked during each lab signoff.
13. **If you are new to soldering, you may want to complete the SMT soldering lab and also do some practice soldering on a scrap PCB before doing any soldering on your board for this course. Ask the instructor for details during lecture.**
14. Insert the wire wrap socket(s) from the top side of the board. Carefully solder the wire wrap sockets to the PCB (be careful not to use too much solder, as you don't want to solder together your power and ground planes by mistake). If you examine the PCB carefully, you'll notice that not all the pins for each chip have electrical connections on the board - the VCC pin, GND pin, and some signal pins on the chips have connections to traces on the PCB. **At a minimum, the VCC and GND pins of each socket must be soldered to the board, as well as the pins which have traces on the board. Make sure you've completed all the soldering before you start wire wrapping to a socket!** It's easy to melt the insulation on the wire wrap wires if you have to come back and solder to the socket after you've already finished your wire wrapping. **Make sure the wire wrap sockets are tight against the board before you start soldering.**
15. You will need to wire up the 2.1mm power jack, a master on/off power switch and +5V regulator. If you plan to use a heat sink on your regulator, be sure to leave enough space on the board. Pay close attention to the polarity of the wall adapter plug. Different plugs have different polarities, and if you're not careful and use the wrong polarity, you can destroy your components on your board. You will use the diode bridge rectifier on your PCB to protect against damage caused by using a power supply with the opposite polarity. Use heavier wire (e.g. 22 AWG) for your main power connections or double up your wire wrap connections. Remember, when you solder circuitry such as the 7805 regulator, be careful about applying too much heat, or you'll end up damaging or destroying the circuitry. If you don't use the diode bridge, clearly label the polarity of your power connection so that you'll always know what kind of adapter to use.

Example: + —  — -

16. You will also want to mount your RS-232 connector at this time. Solder in the 9 pins of the RS-232 connector (reference designator J5). You can also solder in an 8-pin or 9-pin header so that you'll be able to wire wrap to the RS-232 pins later in the semester. If using an 8-pin header, make sure to solder it in to positions 1-8 on the header outline for reference designator J4.
17. The individual T44 wire wrap pins can be used to hold discrete components as necessary.
18. You must choose wire colors to use when implementing your circuits. For this class, red is always used for power and black is always used for ground. Your other connections must be colors other than red or black. You are free to choose whatever other colors you wish; however, remember that when debugging, it is easier when particular wire colors signify a particular type of signal, and when the chosen colors contrast with each other and the background to a great degree. For example, it is very difficult to debug a board when the background is white and when only white wire wrap wire is used for all connections. One color scheme is shown below:

Signal Type	Color	Comment
Power	Red	Must be red
Ground	Black	Must be black
Multiplexed Address/Data	Gray	Your choice of color
Buffered Data	Yellow	Your choice of color
Latched Address	Blue	Your choice of color
Control Signals	Orange	Your choice of color
Serial Port Signals	Green	Your choice of color

19. After you have become proficient at basic wire wrapping technique, it is time to start wire wrapping your base microcontroller board. The strategy often used is first to lay down the wires which are least likely to move or change, so that any wires you have to adjust later are laying on top of the other wires. First hook up all your ground connections. Remember what you learned about loop size and placement of the decoupling capacitors—**keep the caps close to the IC power and ground pins and keep the leads as short as possible**. If you need to solder your decoupling caps into the T44 pins, now is a good time to do this. When wiring, make sure you get good connections so that the sockets are not terribly loose. Leave just a little slack in the wire connections so that you can debug easier later in the semester. If the wires are too tight, then it's difficult to move them when you need to see silkscreen labels or other wires underneath. After you have completed wiring up your ground connections, wire all your +5V connections. Remember to strip at least 3/4" of bare wire in order to wire wrap. 0.75 inches is about this long: 
20. Once you have finished wiring up all your ground and +5V connections and **before turning on power**, you need to test to make sure that you do not have any short circuits. Using a multimeter, test between your +5V and ground connections to verify that there is an open circuit between power and ground. If you catch a mistake at this point, there are fewer wires to search through to find the problem. **Use this approach as you are wiring up your board—take small steps, and verify your work often**. This will save time in the long run.
21. Now, **before** putting in any chips, turn on power and verify that you have +5V and ground at the correct pins on your sockets. Measure the voltage with a digital multimeter. Using the oscilloscope, verify that the VCC voltage is close to 5.0V and looks stable at 5.0V, without big oscillations.
22. Wire up your reset circuitry and your oscillator circuitry, and tie the 8051 \overline{EA} line low. **Keep the oscillator circuitry close to the microcontroller and use very short wires. Pull-up your Port 0 pins to VCC so that the processor doesn't go into power-down mode**. You can use a resistor network in a SIP package or discrete resistors. You may not need to pull up all 8 data lines.
23. If you have verified all the basic connections and circuitry, you can now insert your microcontroller (with the power off). Then, turn on power, and use an oscilloscope verify that your ALE line is oscillating at the correct frequency (1/6 the XTAL2 frequency). Use an oscilloscope to view the XTAL2 waveform and check its frequency. If you want, use a logic analyzer to verify that a fetch

from address 0000h is occurring immediately after the processor comes out of reset. **You need to make sure that your oscillator starts reliably every time power is turned on and after a reset. You may need to adjust the oscillator load capacitance.** Be aware that the oscilloscope probe capacitance can affect your oscillator startup when you probe the XTAL1 and XTAL2 pins.

24. Using the oscilloscope, verify that the VCC voltage is close to 5.0V and that the peak to peak noise between VCC and GND on your C501 is less than ~800mV. If necessary, add more bypass capacitors (1.0uF/4.7uF/etc.) across the C501 power pins.
25. Wire up the '373 latch to the microcontroller.
26. All ICs you add to your board must be labeled with identification of the IC name, pin numbers, and all signal names, similar to the information present on the PCB silkscreen. Wire wrap label templates are available on the course web site (search for "Wire Wrapping ID"), and may be helpful to you for the parts you add (e.g. the SPLD) which don't already have silkscreen present on the PCB.
27. Connect and test your digital logic.
 - a) Wire the Atmel AT16V8C SPLD socket. Attach A15, A14, A13, A12, /RD, and /PSEN from the processor to six of the SPLD inputs (matching the assignments in your WinCUPL code).
 - b) Use digital logic (e.g. program the SPLD) to generate two outputs:
/READ = /RD & /PSEN, and /CSPERIPH = !(A15 & A14 & A13 & A12).
 - c) Verify the SPLD outputs. Examine the /READ output of the SPLD to verify that it is toggling when /PSEN toggles. The /CSPERIPH OUTPUT should be high most of the time, and should have a 15/16 duty cycle (it will be low only for addresses in the range of F000h-FFFFh, while the processor continuously cycles through addresses 0000h to FFFFh).
28. Think carefully about the steps you will need to take to complete your base board, and formulate a plan for incrementally wiring and testing parts of your circuit.
29. Start learning about the EFM8BB1/ARM architecture and using development boards (more guidance will be provided by the instructor and TAs):
 - a) Read about your specific development boards (Silabs EFMBB1LCK and TI MSP432 or STM32 or other). [Some information and links are available via Canvas]
 - b) Set up the development environments, then build and run some sample programs on your development boards. [More information will be provided by the TA's.]
 - c) Explain your key learnings to the TA's.

NOTE: Carefully prepare for your signoff with the TA's. Make sure you are well organized and that you understand the lab material and your implementation completely. Be prepared to demonstrate your skills with the lab equipment and answer questions posed by the TA. Be ready to start your signoff on time. Demonstrate all elements of the lab assignment in a time efficient manner and utilize clear communication.

NOTE: Students must submit their work to be signed off on Canvas by 4pm on the signature due date. Students will sign off using that version of their work and can download that version during their signoff with the TA. This common submission deadline of 4pm has been chosen to ensure that all students have the same amount of time to complete their lab work before it is considered late. If a student makes changes to their design files after the 4pm submission deadline, the date of that new work will be considered to be that student's submission date. To avoid late penalties, all students are encouraged to have their work complete and well commented when they submit it by 4pm on the submission due dates.

SUBMISSION INSTRUCTIONS

Please follow the instructions given below:

1. Create a folder called "lastname_lab_1" where "lastname" is your last name. You will create sub-folders inside this unzipped folder, ending with a folder structure like the following:
 lastname_lab_1
 schematic
 asm_code
 spld_code
 lab_writeup
 arm
 efm8
2. Please include a legible and easy-to-view copy of your schematic in pdf format inside the sub-folder named "schematic". In case you don't have access to pdf writer software, you can download a freeware solution from the following link: <http://www.cutepdf.com/Products/CutePDF/writer.asp> (Links to an external site.)
3. Include all your assembly code files like .asm and .lst in the sub-folder named "asm_code". Ensure that these files are neatly formatted and easy to read.
4. Include your spld source file (i.e. .pld file) and the spld simulation file (i.e. .si file) in the sub-folder named "spld_code".
5. Submit any ARM code you demonstrated in the sub-folder named "arm".
6. Submit any EFM8BB1 code you demonstrated in the sub-folder named "efm8".
7. Submit all the calculations that are required to be done for answering the questions that have been asked in the sign-off sheets or lab assignment. Submit the answers either in Word or PDF format. Include these files in the sub-folder named "lab_writeup". Include the screen-shots (if any) in PDF format in this folder itself. Comment on any significant learnings from the lab assignment.
8. Submit a scan of the duly signed sign-off sheets and the submission sheet in the lab writeup folder. You could choose to include them at the beginning of your write-up document. You must include clear high-resolution pictures of top and bottom sides of the 8051 board you assembled for this lab, including wiring and labels; wire wrapping and soldering should be clearly visible when you zoom in – **make sure your pictures are in focus**. Use JPEG format.
9. Submit a zipped version of the folder "lastname_lab_1" as an attachment via the Canvas interface. Please use only the ".zip" file format when submitting files.
10. Please contact the TA's or instructor in case you have any doubts regarding submissions.

Note:

For the Lab 1 Part 1 Checkpoint Submission:

- ❑ Please upload your .lst file and WinCUPL code file in a zip file in the following format:
 - ❑ The zip file should be named in the following format: "lastname_lab_1_signoff_sw.zip", and must have the .lst and WinCUPL code files inside.
 - ❑ The WinCUPL code file must be placed in the "spld_code" folder, the .lst file must be placed in the "asm_lst" folder.

For the Lab 1 Part 2 Signoff Submission:

- ❑ Please make sure to upload a PDF copy of your schematics.

For the Lab 1 Part 3 Signoff Submission:

- ❑ Please make sure to upload an updated PDF copy of your schematics that accurately represents your actual hardware implementation.

You will need to obtain the signature of your TA on the following items in order to receive credit.

The Part 1 & Part 2 Elements of Lab #1 should be completed and signed off by **Friday, Sept. 15, 2023** in order to give you time to complete the Part 3 Elements upon receipt of your parts kit. All signoffs are due by **Friday, Sept. 22, 2023**. You need to submit both of your signoff sheets and other required elements by **11:59pm Sunday, Sept. 24, 2023**. Labs completed after the signature due date or submitted after the submission due date will usually receive grade reductions, but there is leniency on Lab #1.

Print your name below and then demonstrate your working hardware/firmware in order to obtain the necessary signatures. All items must be completed to get a signature, but partial credit is given for incomplete labs. Receiving a signature on this signoff sheet does not mean that your work is eligible for any particular grade; it merely indicates that you have completed the work at an acceptable level.

Student Name: _____

Checklist

- ☐ Student demonstrates detailed knowledge of an 8051 simulator or debugger (including changing register values, editing data memory, using breakpoints, single stepping, uses /overlay option, etc.)
- ☐ Student assembly program works correctly
- ☐ Student demonstrates detailed knowledge of WinCUPL and WinSim, logic equations correct
- ☐ Student demonstrates detailed knowledge of the final project assignment and discusses any questions with the TAs.

Student Answers to Lab Questions

1. **How many bytes of code space does your program require?**
(Show how you arrived at your answer.)

Code Size? _____

2. **How long did your program take to execute for X=0x93 and Y=0x0A? Assume an 11.0592 MHz clock and include the instructions executed from the beginning until you reach the ENDLOOP label. Show the TA your detailed calculations on the code listing during your signoff.**

Execution Time? _____

Instructor/TA Comments: ☐ ☐ ☐

TA signature and date

<u>FOR INSTRUCTOR USE ONLY</u>	Not Applicable	Poor/Not Complete	Meets Requirements	Exceeds Requirements	Outstanding
SPLD code	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Assembly Language Code Style	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Required Elements functionality	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Sign-off done without excessive retries	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Student understanding and skills	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Overall Demo Quality	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Comments:

NOTE: This submission sheet should be the top/first sheet of your submission.

Print your name below, answer the questions, and then demonstrate your working hardware in order to obtain the necessary signatures. All items must be completed to get a signature.

Student Name: _____

Checklist

- ☐ Schematic of acceptable quality, Student name on board in permanent ink
- ☐ Pins and signals labeled, decoupling capacitors, and two 28-pin wire wrap sockets present on board:
- ☐ Mounting hardware present (e.g. standoffs or an enclosure)
- ☐ Power switch and LED, voltage regulator functional, power jack present
- ☐ Power-on Reset (RC) and Run-time Reset (pushbutton), 8051 bypass cap is present
- ☐ RS-232 connector mounted, 74LS373 transparent latch wired
- ☐ Logic outputs correct (e.g. SPLD generation of /READ and /CSPERIPH; view SPLD code)
- ☐ Student displays good knowledge of oscilloscope
- ☐ Peak to peak noise measured across processor VCC and GND is < 800mV
- ☐ Oscillator functional (check for correct ALE/XTAL2 signals after power on-off cycles)
- ☐ EFM8 & ARM development boards functional, student can demonstrate the basic software.

Student Answers to Lab Questions

1. **What voltage is present at the regulator input?** Use a digital multimeter. _____
2. **What voltage is present at the regulator output?** Use a digital multimeter. _____
3. **What peak to peak noise is present across the processor VCC and GND?** Use an oscilloscope.

Measured value at processor package pins on top side of board: _____

Measured value at wire wrap socket pins on bottom side of board: _____

4. **How long is the processor held in reset after the run-time reset pushbutton is released?** Use an oscilloscope and try to measure the time between the release of the pushbutton and the time when noise from ALE is observed on the RST signal.

Measured value: _____

5. **What frequency is present at the ALE pin?** Use an oscilloscope. _____

Instructor/TA Comments: ☐ ☐ ☐

TA signature and date

<u>FOR INSTRUCTOR USE ONLY</u>	Not Applicable	Poor/Not Complete	Meets Requirements	Exceeds Requirements	Outstanding
Schematics, SPLD code	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Hardware physical implementation	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Required Elements functionality	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Sign-off done without excessive retries	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Student understanding and skills	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Overall Demo Quality	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Comments:

NOTE: This submission sheet should be the second sheet of your submission.

Submission Sheet

Instructions: Print your name below and sign the honor code pledge. Separate the signoff and submission sheets from the rest of the lab and turn in a scan (or clear picture) of these signed forms, the items in the checklist below, and the answers to any applicable lab questions in order to receive credit for your work. No cover sheet please. **Submit all items electronically via Canvas to reduce paper usage. Canvas is <https://canvas.colorado.edu>.**

Remember, in addition to the items listed on the signoff checklist, be sure to review the lab for additional requirements for submission, including:

- ☐ Scan of signed and dated Part 1 & 2 Elements signoff sheet as the top sheet (No cover sheet please)
- ☐ Scan of signed and dated Part 3 Elements signoff sheet as the second sheet
- ☐ Scan of submission sheet with signed honor code pledge as the third sheet
- ☐ PDF of complete and accurate final schematic of acceptable quality (all components shown).
- ☐ Fully, neatly, and clearly commented assembly code.
- ☐ Clear high-resolution pictures of the top and bottom sides of your 8051 board. Must be able to read any silkscreen/labels on the board as well as zoom in and see the solder joints and wire wraps.

Make copies of your code, SPLD code, and schematic files and save them as an archive.

Student Name: _____

Honor Code Pledge: "On my honor, as a University of Colorado student, I have neither given nor received unauthorized assistance on this work. **I have clearly acknowledged work that is not my own.**"

Student Signature: _____

1. **How much power is dissipated in the regulator, assuming a load current of 210mA?** Assume that the regulator is drawing the max quiescent current shown in the data sheet (use the correct data sheet for the regulator you have on your board). Neatly show all your work.

Calculated value: _____

Comments:

NOTE: This submission sheet should be the third sheet of your submission.